

BALLARI INSTITUTE OF TECHNOLOGY & MANAGEMENT

(Autonomous Institute under Visvesvaraya Technological University, Belagavi)

USN

--	--	--	--	--	--	--	--	--	--

Course Code

22CS/AI/CA/CD/32

Third Semester B.E. Degree Examinations, September 2024

DIGITAL SYSTEM DESIGN AND COMPUTER ORGANIZATION

(Common to CSE, AIML, CSE- AI, CSE- DS)

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions choosing ONE full Question from each Module.
2. Missing data, if any, may be suitably assumed

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
<u>Module-1</u>			
1.	<p>a. Find the minimum sum-of-products expression for each function using K-maps:</p> <p>(i) $f(a, b, c, d) = \sum m(0, 2, 3, 4, 7, 8, 14)$</p> <p>(ii) $f(a, b, c, d) = \prod M(1, 2, 3, 4, 9, 15)$</p> <p>b. Find the minimum sum of products and the minimum product of sums for the function using K-maps:</p> <p>$f(a, b, c, d) = \sum M(0, 1, 6, 8, 11, 12) + \sum D(3, 7, 14, 15)$</p>	10	(3 :1: 1.7.1)
(OR)			
2.	<p>a. Find the minimum sum-of-products expression for each function using Quine-McCluskey method:</p> <p>$F(A, B, C, D) = \sum m(2, 3, 4, 7, 9, 11, 12, 13, 14) + \sum d(1, 10, 15)$</p> <p>b. Using the method of map-entered variables, use four-variable maps to find a minimum sum-of-products expression for</p> <p>$F(A, B, C, D, E) = \sum m(0, 4, 6, 13, 14) + \sum d(2, 9) + E(m1 + m12)$</p>	10	(3 :1: 1.7.1)
<u>Module-2</u>			
3.	<p>a. (i) Show how two 2-to-1 multiplexers (with no added gates) could be connected to form a 3-to-1 MUX. Input selection should be as follows:</p> <p>If $AB = 00$, select I_0</p> <p>If $AB = 01$, select I_1</p> <p>If $AB = 1-$ (B is a don't-care), select I_2</p> <p>(ii) Show how two 4-to-1 and one 2-to-1 multiplexers could be connected to form an 8-to-1 MUX with three control inputs.</p> <p>b. Realize a full subtractor using a 3-to-8-line decoder with inverting outputs: (i) Two NAND gates. (ii) Two AND gates.</p>	10	(3 :2: 1.7.1)
(OR)			
4.	<p>a. Design PLA circuit for the following function:</p> <p>$F0 = \sum m(0, 1, 4, 6)$ $F1 = \sum m(2, 3, 4, 6, 7)$ $F2 = \sum m(0, 1, 2, 6)$ $F3 = \sum m(2, 3, 5, 6, 7)$.</p>	10	(3 :2: 1.7.1)

Note: (RBTL - Revised Bloom's Taxonomy Level: CO - Course Outcome: PI- Performance Indicator)

b. Design using **PAL** a Full Adder **10** (3 :2: 1.7.1)

Module-3

5. a. Explain the working of a n-bit parallel adder with accumulator **10** (2 :3: 1.7.1)

b. Design and construct 3bit binary synchronous counter using TFF **10** (3 :3: 1.7.1)

(OR)

6. a. Describe Johnson's counter and Ring counter **10** (2:3: 1.7.1)

b. Design a counter using JK-FF for the sequence 1 →3 → 2 → 6 → 7 → 5 →4→1 **10** (3 :3: 1.7.1)

Module-4

7. a. List basic operational steps of computer for Add LOCA, R0. **10** (2 :4: 1.7.1)

b. Solve and explain $Y = (A+B) * (C+D)$ using one-address, two-address, three-address instructions. **10** (3 :4 :1.7.1)

(OR)

8. a. What is the effective address of the source operand in each of the following instructions, when the Register R1, and R2 of computer contain the decimal value 2300 and 3200? **10** (3 :4: 1.7.1)

(i) Load 50(R1), R5 (ii) Move #2000, R5 (iii) Store 40(R1, R2), R5 (iv) Add -(R1), R2 (v) Subtract (R2) +, R5.

b. Explain factors affecting performance of the computer? Give basic performance equation and overall SPEC rating of computer. **10** (2 :4: 1.7.1)

Module-5

9. a. Solve following numbers representing by 5 bits: **10** (3 :5: 1.7.1)

(i) (-4) + (6) (ii) (-3) - (-7) (iii) (5) - (9) (iv) (8) +(-5)

b. What is Interrupt, ISR and Vectored Interrupts? Illustrate with example. **10** (2 :5: 1.7.1)

(OR)

10 a. Apply booth algorithm to perform the multiplication on -11 and +07. **10** (3 :5: 1.7.1)

b. Write a program to illustrate reading one line from keyboard, storing into memory and echoing back to the display. **10** (3 :5: 1.7.1)

** ** *