

BALLARI INSTITUTE OF TECHNOLOGY & MANAGEMENT

(Autonomous Institute under Visvesvaraya Technological University, Belagavi)

USN

--	--	--	--	--	--	--	--	--	--

Course Code

2	1	C	S	3	4
---	---	---	---	---	---

Third Semester B.E. Degree Examinations, April/May 2023

DIGITAL SYSTEM DESIGN AND COMPUTER ORGANIZATION

(Common to CSE & AIML)

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
<u>MODULE – 1</u>			
1.	a. Solve the following functions using K-Map to find minimum SOP. Also list all essential prime implicants. $f(A, B, C, D) = \sum m(1, 3, 4, 11) + d(2, 7, 8, 12, 14, 15)$	10	(3 : 1 : 1.7.1)
	b. Solve the following functions using K-Map to find minimum POS. Also list all essential prime implicants. $f(A, B, C, D) = \prod M(0, 1, 6, 8, 11, 12) \cdot \prod D(3, 7, 14, 15)$	10	(3 : 1 : 1.7.1)
OR			
2.	a. Find all prime implicants using Quine McCluskey method and list all essential prime implicants using implicant chart. $F(a, b, c, d) = \sum m(0, 1, 3, 5, 6, 7, 8, 10, 14, 15)$	10	(3 : 1 : 1.7.1)
	b. Using Map entered variable use four variable map to find minimum SOP $Z(a, b, c, d, e, f, g) = \sum m(0, 3, 13, 15) + \sum d(1, 2, 7, 9, 14)$	10	(3 : 1 : 1.7.1)
<u>MODULE – 2</u>			
3.	a. What is multiplexer? Design 8:1 MUX using two 4:1 mux and one 2:1 Mux.	06	(3 : 2 : 1.7.1)
	b. What is Decoder? Realize full adder using 3:8 line decoders using: (i) Two OR gates (ii) Two NOR gates	07	(3 : 2 : 1.7.1)
	c. Design PLA circuit for the following function: $F0 = \sum m(0, 1, 4, 6)$ $F1 = \sum m(2, 3, 4, 6, 7)$ $F2 = \sum m(0, 1, 2, 6)$ $F3 = \sum m(2, 3, 5, 6, 7)$	07	(3 : 2 : 1.7.1)
OR			
4.	a. Implement full adder and full subtractor using a PAL.	10	(3 : 2 : 1.7.1)
	b. Derive characteristics equation for J K Flip-Flop, S R Flip-Flop, D Flip-Flop, and T Flip-Flop.	10	(3 : 2 : 1.7.1)
<u>MODULE – 3</u>			
5.	a. Explain 8-bit serial-in, serial-out shift register using S R Flip-Flop.	10	(2 : 3 : 1.7.1)
	b. Construct MOD-5 counter using J K Flip-Flop.	10	(3 : 3 : 1.1.1)
OR			
6.	a. Construct counter using JK Flip-Flop for the following counting sequence $000 \rightarrow 100 \rightarrow 111 \rightarrow 010 \rightarrow 011 \rightarrow 000$	10	(3 : 3 : 1.7.1)
	b. Explain a short note on : (i) Sequential parity checker (ii) Register transfers	10	(2 : 3 : 1.7.1)

MODULE – 4

- | | | | | |
|----|----|--|----|----------------|
| 7. | a. | Explain basic operational concepts with neat diagram and example. | 08 | (2 :4 : 1.7.1) |
| | b. | What is performance? Give basic performance equation and overall SPEC rating of computer. | 08 | (2 :4 : 1.7.1) |
| | c. | Explain Big-Endian and Little-Endian. Show the content of the two memory words at address 1000 and 1004 for the name “johnson” has been entered in both methods. | 04 | (2 :4 : 1.7.1) |

OR

- | | | | | |
|----|----|--|----|----------------|
| 8. | a. | Explain any 4 addressing modes with an example. | 08 | (2 :4 : 1.7.1) |
| | b. | Explain basic instruction types with an example. | 07 | (2 :4 : 1.7.1) |
| | c. | What is Branching? Explain with an example. | 05 | (2 :4 : 1.7.1) |

MODULE – 5

- | | | | | |
|----|----|--|----|----------------|
| 9. | a. | Explain handling multiple devices simultaneous request(daisy chain, arrangement of priority groups) | 08 | (2 :5 : 1.7.1) |
| | b. | Construct a program that reads a line of characters and display it. | 05 | (3 :5 : 1.7.1) |
| | c. | What is DMA? What are it advantages? With supporting diagram, explain different registers used in DMA interface. | 07 | (2 :5 : 1.7.1) |

OR

- | | | | | |
|-----|----|--|----|----------------|
| 10. | a. | Explain addition and subtraction of signed numbers using 2s compliment method with an example.
(i) -5 and 7 (ii) -3 and -8 | 06 | (2 :5 : 1.7.1) |
| | b. | Construct 4 bit Carry Look Ahead adder, and unit the expression for C_{i+1} . And compare its performance with Ripple Bit Carry adder. | 07 | (3 :5 : 1.7.1) |
| | c. | Explain booth algorithm to perform the multiplication on +13 and -06. | 07 | (2 :5 : 1.7.1) |

**** ** ***