

Basavarajeswari Group of Institutions
BALLARI INSTITUTE OF TECHNOLOGY & MANAGEMENT
 (Autonomous Institute under Visvesvaraya Technological University, Belagavi)

USN

--	--	--	--	--	--	--	--	--	--

Course Code

2	1	E	C	3	4
---	---	---	---	---	---

Third Semester B.E. Degree Examinations, September / October 2024

ANALOG ELECTRONIC CIRCUITS

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
MODULE – 1			
1.	a. Describe the characteristics of pn-junction with necessary equations.	06	(1 : 1 : 1.3.1)
	b. Explain the half wave rectifier with circuit diagram, necessary waveforms and calculate efficiency for the same.	08	(2 : 1 : 1.3.1)
	c. Explain the construction and operation of Bipolar Junction Transistor (BJT) with carrier flow diagram.	06	(2 : 1 : 1.3.1)
OR			
2.	a. Explain in detail about the negative series clipper with circuit diagram and necessary waveform.	04	(1 : 1 : 1.3.1)
	b. Define voltage regulator and explain different types of voltage regulators.	10	(2 : 1 : 1.3.1)
	c. Explain the construction and operation of MOSFET.	06	(2 : 1 : 1.3.1)
MODULE – 2			
3.	a. Explain the voltage divider biasing for BJT using a single power supply. How does R_E provide a negative feedback action to stabilize the bias current with necessary supporting mathematical equations?	08	(2 : 2 : 1.3.1)
	b. Draw the small signal equivalent circuit model for MOSFET and obtain the expression for voltage gain and transconductance.	08	(2 : 2 : 1.3.1)
	c. A BJT having $\beta=120$ is biased at DC collector current of 1mA. Find the Value of g_m , r_e and r_π at the bias point.	04	(3 : 2 : 2.1.2)
OR			
4.	a. Explain biasing of MOSFET by fixing V_{GS} .	04	(2 : 2 : 1.3.1)
	b. Derive the following relation with respect to small signal operation of BJT: (i) Input resistance (ii) Emitter resistance Also derive the relation between emitter and base resistance.	08	(2 : 2 : 1.3.1)
	c. For the circuit shown in Fig. Q4 (c), find the required value of V_{GS} to establish a dc bias current $I_D = 0.5$ mA. Device parameters are: $V_t=1V$, $K_n' \left(\frac{W}{L} \right) = 1$ mA/V ² and $\lambda=0$. What is the percentage change in I_D obtained when transistor is replaced with another having $V_t = 1.5V$.	08	(3 : 2 : 2.1.2)

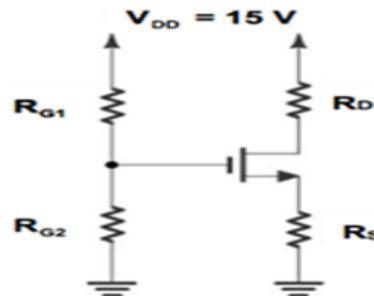


Fig. Q4(c)

MODULE – 3

5. a. With the neat circuit diagram and AC equivalent circuit, derive the expression for R_{in} , A_{vo} , A_v and R_o for a source follower. **08** (2 : 3 : 1.3.1)
- b. With mathematical equations, explain the different internal capacitances in the MOSFET. **06** (2 : 3 : 1.3.1)
- c. For the n-channel MOSFET with $t_{ox}=10$ nm, $L=1\mu\text{m}$, $W=10\mu\text{m}$, $L_{OV} = 0.05\mu\text{m}$, $C_{sbo} = C_{dbo}=10$ pF, $V_O = 0.6$ V, $V_{SB} = 1$ V and $V_{DS} = 2$ V. Calculate i) C_{OX} ii) C_{OV} iii) C_{gs} iv) C_{gd} v) C_{sb} vi) C_{db} **06** (3 : 3 : 2.1.2)

OR

6. a. A Common Source amplifier utilizes a MOSFET biased at $I_D=0.25$ mA with $V_{OV}=0.25$ V and $R_D=20$ K Ω . The device has $V_A= 50$ V. The amplifier is fed with source having $R_{sig}=100$ K Ω and a 20 K Ω load is connected to the output. Find R_{in} , A_{vo} , G_v , A_v and R_o . If to maintain reasonable linearity, the peak of the input sine wave signal is limited to 10% of $(2V_{ov})$ what is the peak of the sine wave voltage at the output? **10** (2 : 3 : 2.1.2)
- b. Write a Short note on: (i) Current Source (ii) Current Mirror **10** (3 : 3 : 1.3.1)

MODULE – 4

7. a. Determine the voltage gain, input and output impedance with feedback for a voltage series feedback amplifier having $A= -100$, $R_i=10$ K Ω , $R_o=20$ K Ω for the feedback of (i) $\beta= 1$ and (ii) $\beta= -0.5$. **10** (3 : 4 : 2.1.2)
- b. Explain the four basic Feedback topologies. **10** (2 : 4 : 1.3.1)

OR

8. a. Explain the operation of Class B amplifier. Prove that the maximum conversion efficiency of Class B transformer coupled amplifier is 78.5%. **10** (3 : 4 : 1.3.1)
- b. What is output stage and discuss the classification of output stages based on the Collector current? **10** (2 : 4 : 1.3.1)

MODULE – 5

9. a. What is an instrumentation amplifier? Explain an instrumentation amplifier. **10** (2 : 5 : 1.3.1)
- b. Explain the operation of monostable multivibrator with relevant diagram and waveform. **10** (2 : 5 : 1.3.1)

OR

10. a. What is R-2R network type DAC? Explain with relevant expression. **10** (2 : 5 : 1.3.1)
- b. Design an Astable Multivibrator using 555 timer with **10** (2 : 5 : 1.3.1)
- (i) $f_0 = 1$ kHz and Duty Cycle = 40% (ii) $f_0 = 2$ kHz and Duty Cycle = 50% (iii) $f_0 = 1$ kHz and Duty Cycle = 70%
- Assume $C = 0.01\mu\text{F}$ for all cases.

** ** *