

USN

--	--	--	--	--	--	--	--	--	--

Course Code

2	2	E	E	3	6	1
---	---	---	---	---	---	---

Third Semester B.E. Degree Examinations, September 2024

ELECTRIC CIRCUIT ANALYSIS

Duration: 3 hrs

Max. Marks: 100

Note: 1. Answer any FIVE full questions choosing ONE full Question from each Module.
2. Missing data, if any, may be suitably assumed

<u>Q. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
--------------	-----------------	--------------	---------------------

Module-1

- | | | | |
|----|---|----|-----------------|
| 1. | <p>a. Explain the following network terminology
(i) network element (ii) branch (iii) node (iv) Mesh</p> <p>b. Using source transformation and source shifting techniques find the voltage across 2Ω resistance as shown in Fig. Q1(b).</p> | 08 | (2 : 1 : 1.3.1) |
| | | 12 | (3 : 1 : 2.1.2) |

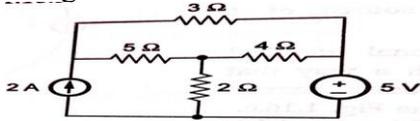


Fig. Q1(b)

(OR)

- | | | | |
|----|---|----|-----------------|
| 2. | <p>a. Derive the delta connected impedance in to its equivalent star connected impedances.</p> <p>b. Write the mesh current for the circuit as shown in Fig. Q2(b) below and determine the mesh currents using mesh analysis.</p> | 08 | (3 : 1 : 1.3.1) |
| | | 12 | (3 : 1 : 2.1.2) |

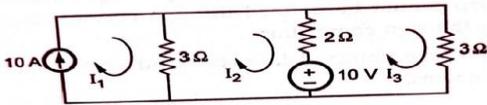


Fig. Q2(b)

Module-2

- | | | | |
|----|--|----|-----------------|
| 3. | <p>a. State and explain the superposition theorem.</p> <p>b. Determine the current I in the network shown in the Fig. Q3(b) and verify the reciprocity theorem</p> | 06 | (2 : 2 : 1.3.1) |
| | | 07 | (3 : 2 : 2.1.2) |

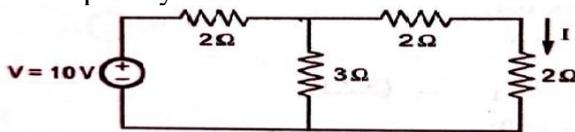


Fig. Q3(b)

- | | | | |
|----|--|----|-----------------|
| c. | <p>For the network shown in the Fig Q3(c), determine the current through R_L using Thevenin's theorem</p> | 07 | (3 : 2 : 2.1.2) |
|----|--|----|-----------------|



Fig. Q3(c)

(OR)

- | | | | |
|----|---|----|-----------------|
| 4. | <p>a. State and explain Norton's theorem.</p> <p>b. Using Millman's theorem find the current through $(2+j3)\Omega$ for the circuit as shown in the Fig. Q4(b) below</p> | 06 | (2 : 2 : 1.3.1) |
| | | 07 | (3 : 2 : 2.1.2) |

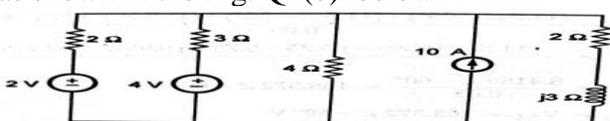


Fig. Q4(b)

- c. Find the value of Z_L for which maximum power transfer occurs in the circuit as shown in the Fig. Q4(c) below. Also find the maximum power delivered to load. **07** (3 : 2 : 2.1.2)

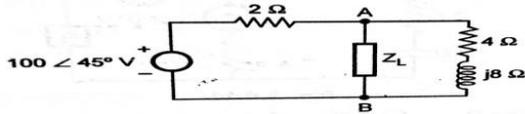


Fig. Q4(c)

Module-3

5. a. Explain (i) Oriented graph (ii) Tree (iii) Fundamental cutset (iv) Fundamental tie set **06** (2 : 3 : 1.3.1)
- b. For the network shown in Fig. Q5(b) draw the dual circuit also write the nodal equation for the dual circuit **07** (3 : 3 : 2.1.2)

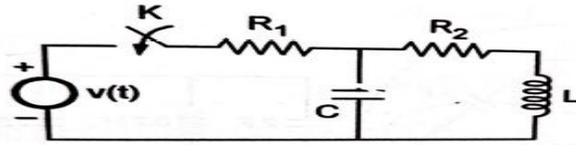


Fig. Q5(b)

- c. A series connected RLC circuit has $R=4\ \Omega$, $L=25\ \text{mH}$. Determine the value of C such that $Q=50$. Also find resonant frequency, band width and half power frequencies. **07** (2 : 3 : 1.3.1)

(OR)

6. a. Derive the expression for resonant frequency for the parallel circuit where R_L - resistance in the inductor branch and R_c = resistance in the capacitor branch. **06** (2 : 3 : 1.3.1)
- b. Two coils: One of $R_1= 0.51\ \Omega$, $L_1= 32\ \text{mH}$ and other coil of $R_2=1.3\ \Omega$, $L_2= 15\ \text{mH}$, are in series and are in series with a capacitor of 25×10^{-6} Farad and 25×10^{-6} Farad and a series resistor of resistance $0.24\ \Omega$. Determine (i) Resonant frequency (ii) Q- factor of the circuit (iii) Bandwidth (iv) Power dissipated in the circuit at resonant frequency **06** (3 : 3 : 2.1.2)
- c. Find the value of R_1 such that the circuit given in the Fig. Q6 (c) resonant **07** (3 : 3 : 2.1.2)

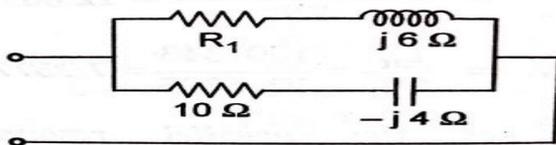


Fig. Q6 (c)

Module-4

7. a. Why do we need to study the initial condition and write the equivalent form of the elements in terms of the initial condition of the element? **06** (2 : 4 : 1.3.1)
- b. Show that the voltage across the capacitor and current across the inductor cannot change instantaneously. **06** (2 : 4 : 1.3.1)
- c. In the circuit shown in Fig. Q7 (c) switch K is changed from position 1 to 2 at $t=0$ steady state condition having reached before swathing find i , di/dt and d^2i/dt^2 at $t=0^+$ **08** (3 : 4 : 2.1.2)

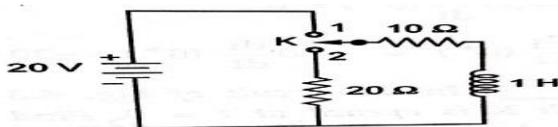


Fig. Q7 (c)

(OR)

8. a. State and prove (i) Initial value theorem (ii) Final value theorem as applied to Laplace transform **06** (2 : 4 : 1.3.1)

- b. Use initial and final value theorems where they apply to find $f(0)$ and $f(\infty)$. 06 (3 :4 : 2.1.2)

$$F(S) = S^3 + 7S^2 + 5 / S(S^3 + 3S^2 + 4S + 2)$$

- c. Obtain the Laplace transform of $f(t)$ for the waveform shown in Fig. Q 8 (c) 08 (3 :4 : 2.1.2)

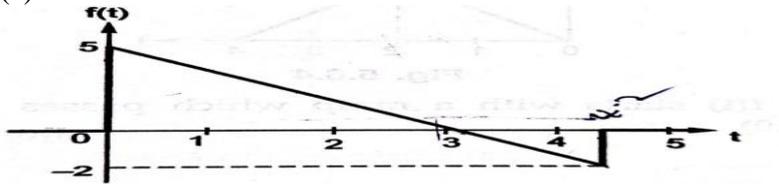


Fig. Q8 (c)

Module-5

9. a. Obtain Z-parameters in terms of y-parameters and transmission parameters. 10 (2 :5 : 1.3.1)
 b. For the network shown in the Fig. Q9 (b), find Z- parameters. 10 (3 :5 : 2.1.2)

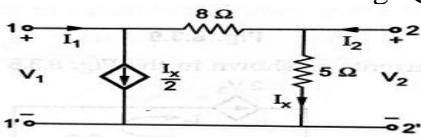


Fig. Q9 (b)

(OR)

- 10 a. Derive transmission line parameters of two port network. 10 (2 :5 : 1.3.1)
 b. Determine the ABCD parameters for the network shown in Fig. Q10 (b) 10 (3 :5 : 2.1.2)

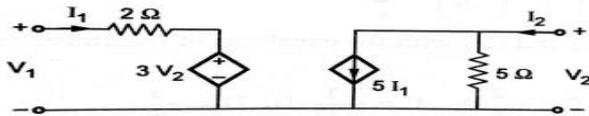


Fig. Q10 (b)

* * * * *