

USN

--	--	--	--	--	--	--	--

Course Code

2	1	E	E	3	2
---	---	---	---	---	---

Third Semester B.E. Degree Examinations, April/May 2023
ELECTRIC CIRCUIT ANALYSIS

Duration: 3 hrs**Max. Marks: 100**

Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
 2. Missing data, if any, may be suitably assumed

<u>O. No</u>	<u>Question</u>	<u>Marks</u>	<u>(RBTL:CO:PI)</u>
MODULE – 1			
1. a.	Define (i). Active and passive elements (ii). Distributed and lumped networks with examples.	06	(2 :1 : 1.3.1)
b.	Determine currents i_1, i_2, i_3 for the circuit shown in Fig. Q1 (b) using mesh analysis.	06	(2 :1 : 1.3.1)

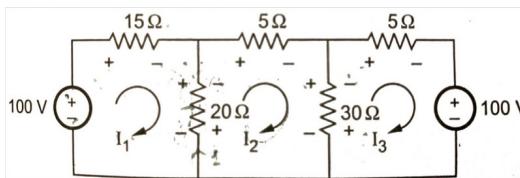


Fig.Q1(b)

- c. Derive three star connected impedances into its equivalent delta connected impedances.

OR

2. a. Find voltage across 2Ω resistor using source transformation and source shifting techniques as shown in Fig. Q2 (a).

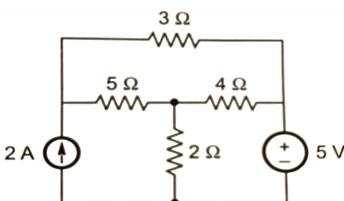


Fig. Q2(a)

- b. Explain how to measure AC and DC quantities using oscilloscope.
 c. Obtain node voltages V_1, V_2 for the network shown in Fig. Q2 (c) using node analysis.

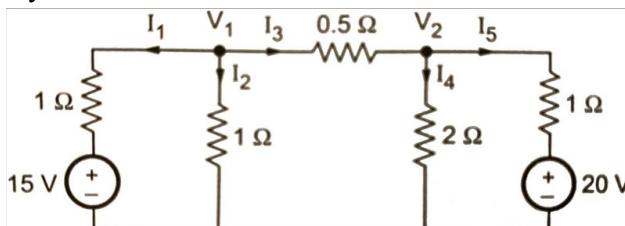


Fig. Q2 (c)

MODULE – 2

3. a. State and prove superposition theorem. Also verify the theorem.
 b. State and prove maximum power transfer theorem for resistive loads.

10 (3 :2 : 1.3.1)

10 (3 :2 : 1.3.1)

OR

4. a. Show that Norton's theorem is dual of Thevenin's theorem. 10 (3 : 2 : 1.3.1)
 b. Find current through load resistance of $10\ \Omega$ for the network shown in Fig. Q4 (b) using Millman's theorem. 10 (3 : 2 : 1.3.1)

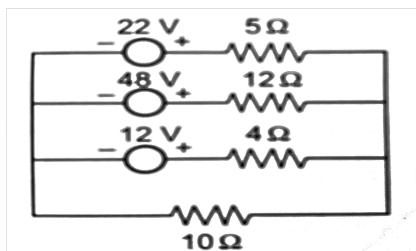


Fig. Q4 (b)

MODULE – 3

5. a. Define graph, tree, co-tree and incidence matrix with examples. 08 (2 : 3 : 1.3.1)
 b. Obtain tie-set schedule and find all the branch currents for the network shown in Fig. Q5 (b). 12 (3 : 3 : 1.3.1)

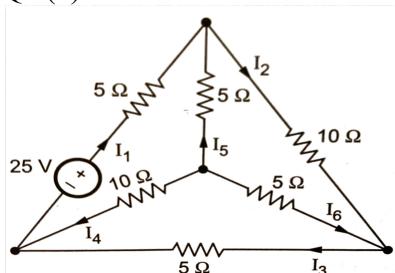


Fig. Q5 (b)

OR

6. a. Derive resonant frequency for both series and parallel RLC circuit. 10 (2 : 3 : 1.3.1)
 b. Show that resonant frequency is geometric mean of two half power frequencies. 10 (3 : 3 : 1.3.1)

MODULE – 4

7. a. For the circuit shown in Fig. Q7 (a), switch 'K' is closed at $t=0$. Find $i(t)$, and $di(t)/dt$ at $t=0^+$. 10 (3 : 4 : 1.3.1)

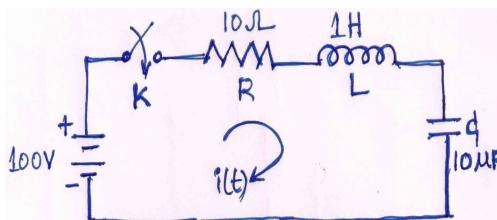


Fig. Q7(a)

- b. Find the values of $i(t)$, $di(t)/dt$ and $d^2i(t)/dt^2$ at $t=0^+$ for the network shown in Fig. Q7 (b) when switch 'K' is moved from 1 to 2. 10 (3 : 4 : 1.3.1)

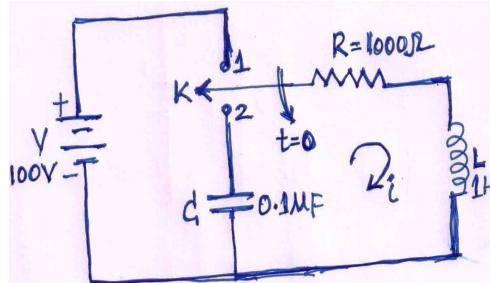


Fig. Q7(b)

OR

8. a. State and prove initial and final value theorem. 10 (3 : 4 : 1.3.1)

Note: (RBTL - Revised Bloom's Taxonomy Level: CO - Course Outcome: PI - Performance Indicator)

- b. Obtain the Laplace transform of the square wave as shown in Fig. Q8 (b). **10** (3 : 4 : 1.3.1)

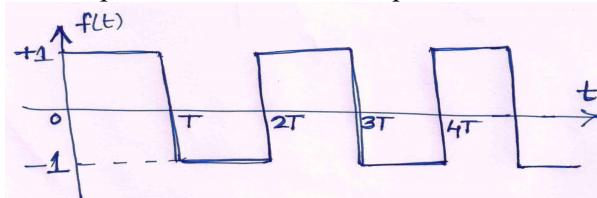


Fig. Q8 (b)

MODULE – 5

9. a. Determine Z and Y parameters for the network shown in Fig. Q9 (a). **10** (3 : 5 : 1.3.1)

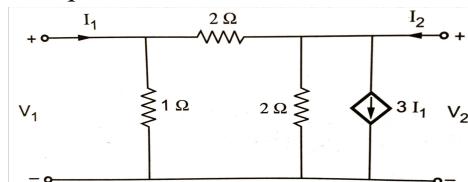


Fig. Q9 (a)

- b. Determine ABCD parameters of given network as shown in Fig. Q9 (b). **10** (3 : 5 : 1.3.1)

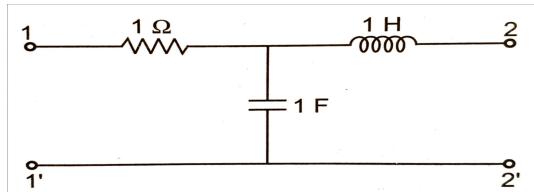


fig.(i)

OR

10. a. Obtain Y-parameters in terms of Z-parameters. **10** (3 : 5 : 1.3.1)
 b. Two identical networks as shown in Fig. Q10 (b) are connected in cascade. Determine the overall transmission parameters of combined network. **10** (3 : 5 : 1.3.1)

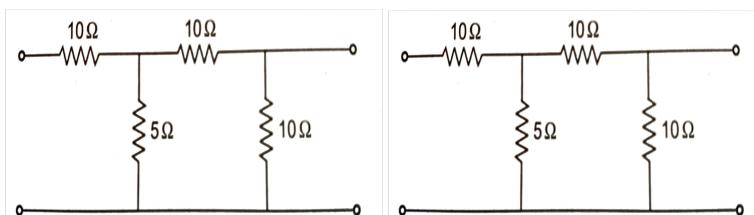


Fig. Q10 (b)

*** * ***